



American International University-Bangladesh

Faculty of Science and Technology

Project Presentation

Spring 2024-25

Introduction to Electrical Circuits LAB

Section : O

Group : 1

Faculty : Sadia Rakinur Rab

Project Title:
Laser Security Alarm using LDR
and Transistor.



Group Members

Md. Sobahan Hasan Saikat 23-52316-2

Kamrun Nahar Mahi 23-52309-2

Abdun Nur Nafis 22-49050-3

Md. Hafiz Sarkar 23-53230-3



Jafrin Khan Bushra 24-56383-1



Objectives

This project utilizes

- Photosensitivity of the LDR for detecting light.
- Voltage divider rule for analog signal control.
- Transistor switching for digital control of output devices like buzzers.




Theory and Methodology

- Laser shines on LDR to keep resistance low.
- Beam interrupted → LDR resistance increases → transistor activates buzzer.

Concepts used:

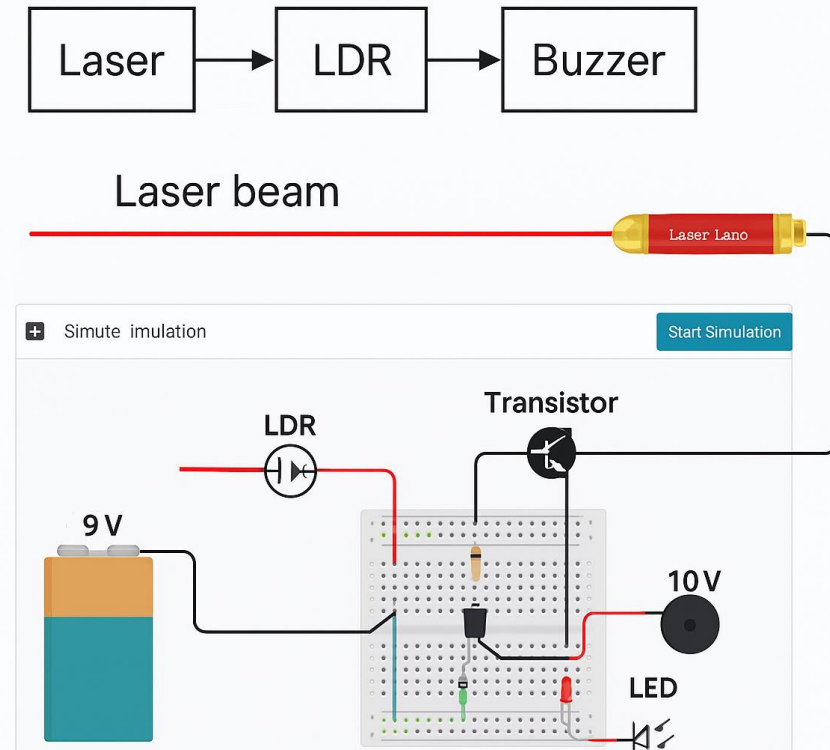
1. LDR (Light Dependent Resistor)
2. Transistor (BC547) switching
3. Voltage divider




Process of Laser Security Alarm

Equipment

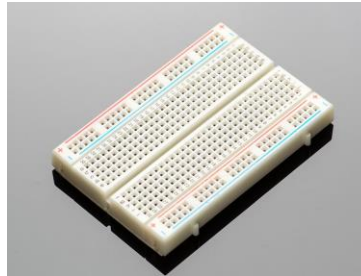1. 9V DC Battery
2. Breadboard
3. Laser Light
4. LDR
5. 10k Ω Resistor
6. BC547 NPN Transistor
7. Buzzer
8. LED
9. Connecting wires



Circuit Diagram

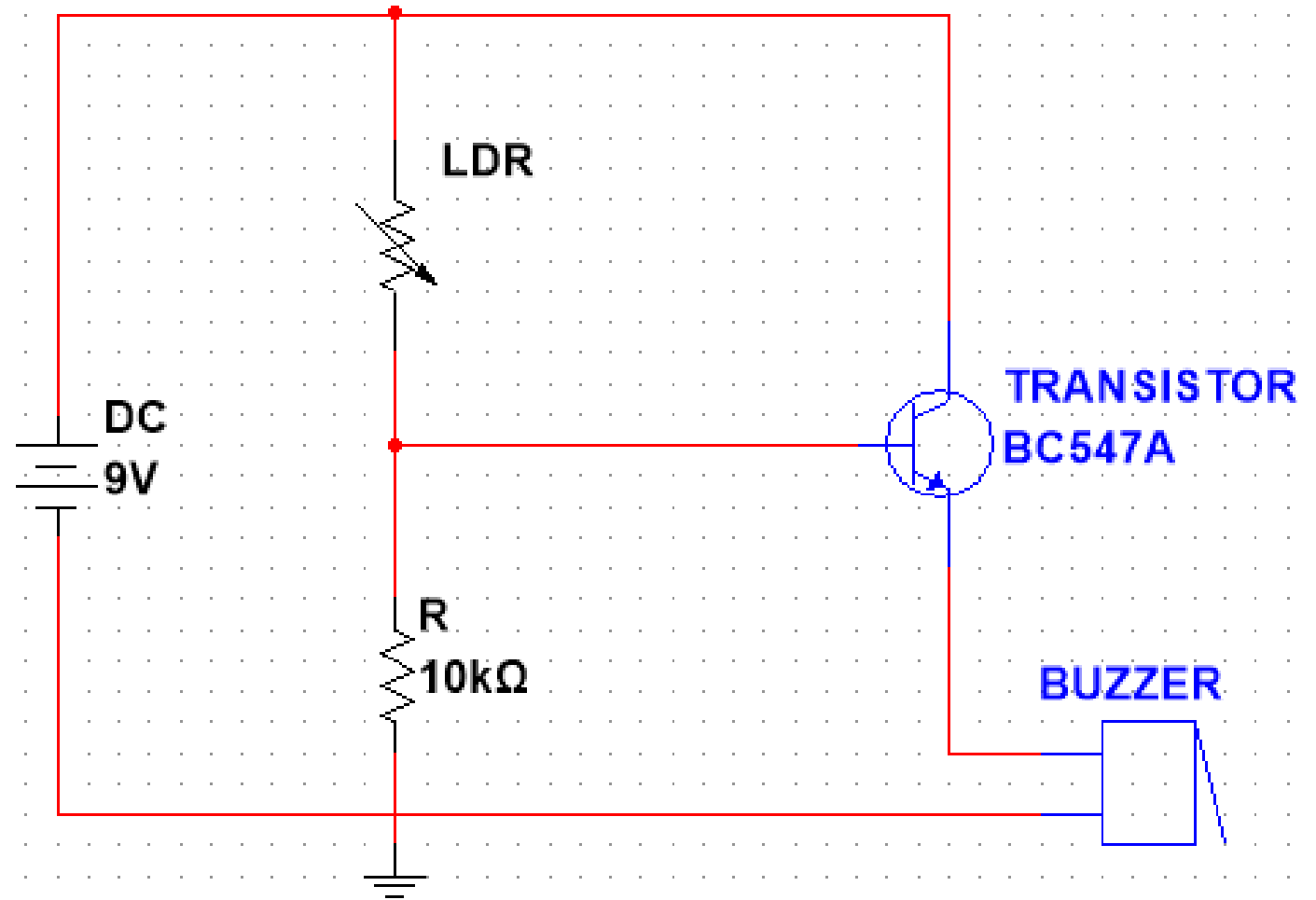

Procedure

Power Source

- 9V battery connected via clip to breadboard

Voltage Divider Setup

- LDR + $10k\Omega$ resistor in voltage divider
- LDR $\rightarrow$ 9V DC
- LDR-Resistor junction $\rightarrow$ BC547 base
- Resistor $\rightarrow$ GND

Transistor Connection

- BC547 emitter $\rightarrow$ GND
- Collector $\rightarrow$ Buzzer (one end)
- Buzzer other end $\rightarrow$ +9V

Operation

- Laser aimed at LDR (constant light)
- Interruption of beam $\rightarrow$ Buzzer activates

Data and Analysis

CONDITION	LDR RESISTANCE	V _{BASE} (APPROX)	TRANSISTOR STATE	BUZZER
Laser on LDR	~ 1kΩ	~ 8.2V	OFF	Silent
Laser interrupted	~ 100kΩ	~ 0.V	ON	ON

LDR Resistance Changes

Voltage Divider Formula,

$$V_{out} = V_{in} \times \frac{R_2}{R_1+R_2}$$

Here,

$$R_1 = \text{LDR}, R_2 = 10\text{k}\Omega, V_{in} = 9\text{V}$$



Example Calculation (Laser Block),

$$\begin{aligned} V_{out} &= 9 \times \frac{10\text{k}}{100\text{k}+10\text{k}} \\ &= 9 \times 0.090982 \text{ V} \\ &= 0.7 \text{ V} \end{aligned}$$

When $V_{base} < 0.7\text{V}$, the transistor turns ON, and the buzzer Sounds.

Simulation

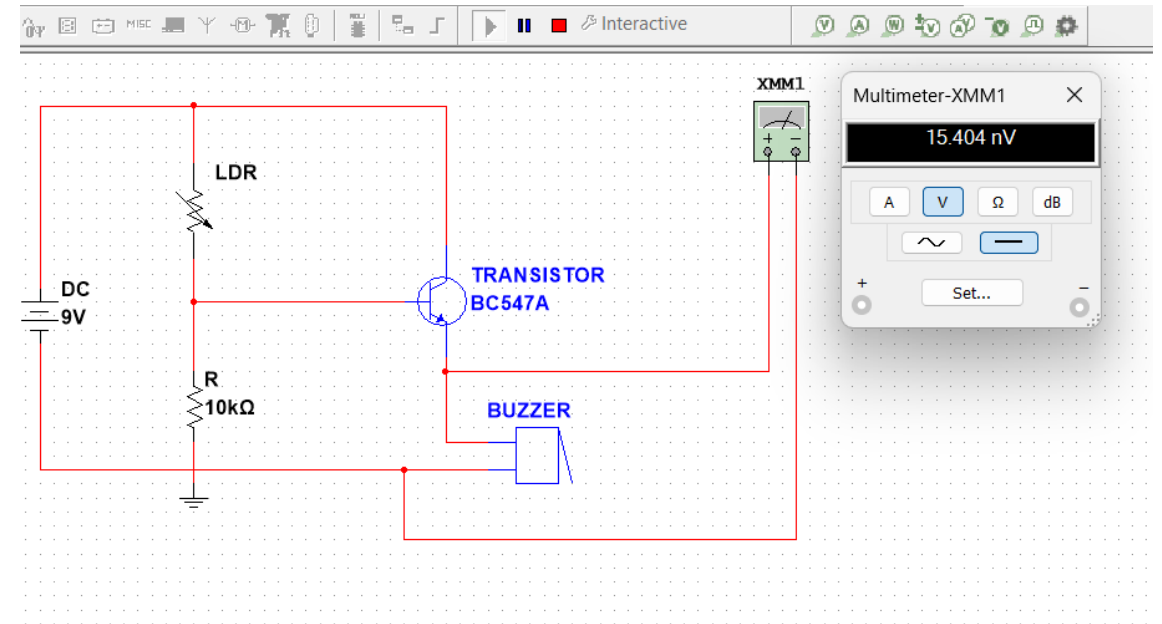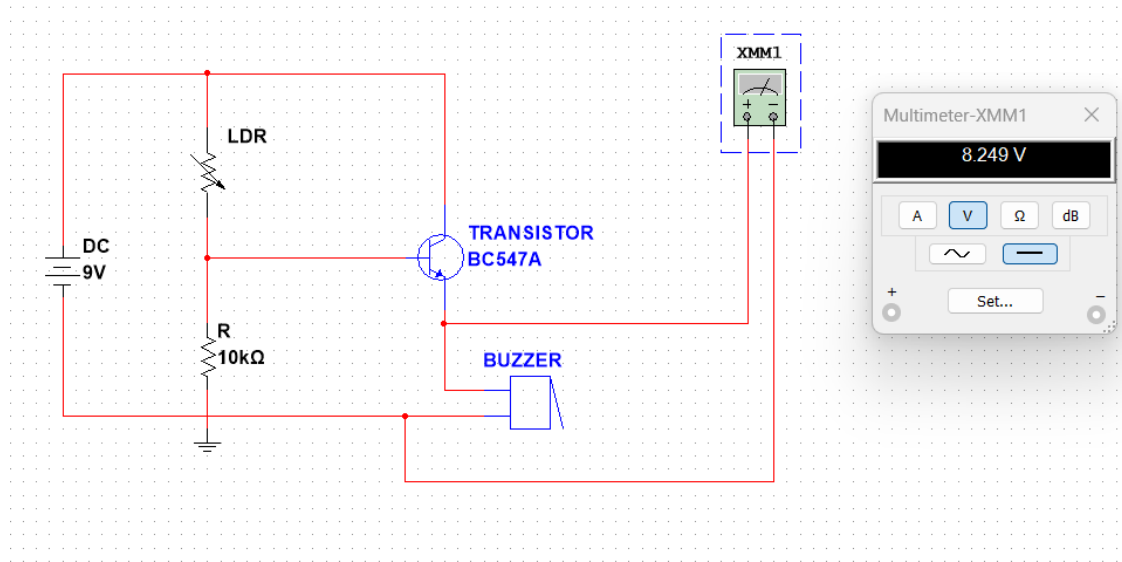LDR's Resistance increases $\Rightarrow$ Turn on Transistor Switch $\Rightarrow$ Buzzer Active



LDR is exposed to the laser, its resistance is low

Discussion

**Pros:**

Simple, sensitive, low cost

**Cons:**

Affected by ambient light, laser alignment, not weatherproof

**Improvements:**

Light shielding, comparator IC

**Uses:**

Security systems, Arduino-based monitoring, area coverage with multiple setups

Conclusion




Effective low-cost security solution.



Demonstrates sensor-based control.



Useful in real-world alarm systems.

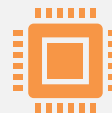

Enhances understanding of transistor switching.



THANK YOU!



ANY QUESTIONS?